



Circuit Basics

[Raspberry Pi](#)[Arduino](#)[DIY Electronics](#)[Programming](#)[Videos](#)[Resources](#)

A COMPLETE GUIDE TO DESIGN AND BUILD A HI-FI LM3886 AMPLIFIER

Posted by Circuit Basics | DIY Electronics | 44



Note: Editable PCB files are available for this project [here](#).

The LM3886 is one of the most highly regarded audio chip amplifiers in the DIY community. The reason for its popularity is due to its very low distortion, minimal external components, and low

Low Cost PCB Prototype


Only **\$2** /10pcs

2-3 days build time >> JLPCB.COM

JLPCB is the largest PCB prototype enterprise in China with 290,000+ customers worldwide and 8000+ online orders per day.

SEARCH ...

cost. With the right layout and component selection, you can build an excellent sounding Hi-Fi audio amplifier that will rival high-end amps retailing for several thousand dollars or more.




Alibaba Cloud Computing


Get \$300 New User Free Credit Now

In this tutorial, I'll go step by step through the amplifier design process as I build a 40 Watt stereo amplifier using [the LM3886](#). I'll explain what each part of the circuit does, and show you how to calculate the right component values with examples from the amplifier I'm building. I'll also show you how to layout the PCB and wire the amplifier in an enclosure for minimal noise and hum.

My amplifier is based off of the same circuit provided in the datasheet, with all of the optional stability components included.

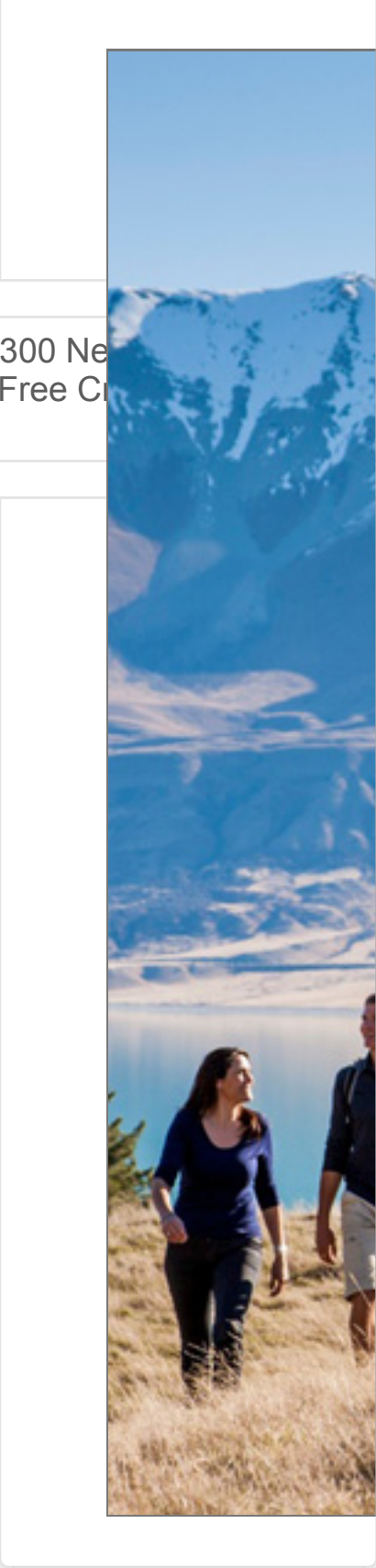BONUS: [Download my parts list](#) to see the components I used to get great sound quality from this amplifier. I've also included the schematic and Gerber files for the power supply I used.





Alibaba Cloud Computing

Get \$300 New User Free Credit Now

I highly recommend reading the datasheet before

building your amplifier. It has all of the performance specifications, absolute maximum ratings, schematics, and design tips:

[LM3886 Datasheet](#)

Application note AN-1192 has additional information that fills in gaps left out of the datasheet. It also has schematics for bridged and parallel amplifier circuits:

[Overture Application Note AN-1192](#)

It's also good to have the Overture Design Guide. This is an Excel spreadsheet that calculates output power, heat sink size, gain, and other useful parameters:

[Overture Design Guide](#)


Since this is a rather long article, here are links to the different sections:

- [Things to Decide Before Starting](#)
- [Determine the Required Power Supply Voltage and Power](#)
 - [Required Power Supply Voltage](#)
 - [Find the Peak Output Voltage](#)
 - [Find the Maximum Supply Voltage Needed by the Amplifier](#)
 - [Find the Maximum Supply Voltage Output by a Transformer](#)
 - [Find the Output Power from a Transformer's Voltage Rating](#)
 - [Required Transformer Power](#)
 - [Convert the Total Power to a Transformer VA Rating](#)
 - [Determine the Proper Heat Sink Size](#)

- Find the Maximum Power Dissipation
- Find the Maximum Thermal Resistance of the Heat Sink
- Calculating the Component Values
 - Find the Minimum Gain Required
 - Setting the Gain
 - Balancing the Input Bias Current
 - Set the Low Frequency Cutoff at the Amplifier's Input
 - Set the Low Frequency Cutoff at the Feedback Loop
 - Set the High Frequency Cutoff at the Amplifier's Input
 - Stability Components R_{f2} and C_f
 - The Zobel Network
 - The Thiele Network
 - Making the Inductors
 - Power Supply Decoupling Capacitors
 - The Mute Circuit
- The Final Schematic
- Designing the Ground Layout
- Designing the PCB Layout
 - Ordering PCBs
 - PCB Design Guidelines
- Wiring it All Together
 - Solder and Soldering
 - Finding a Chassis
 - Wiring Layout Inside the Chassis
 - The Ground Loop Protection Circuit





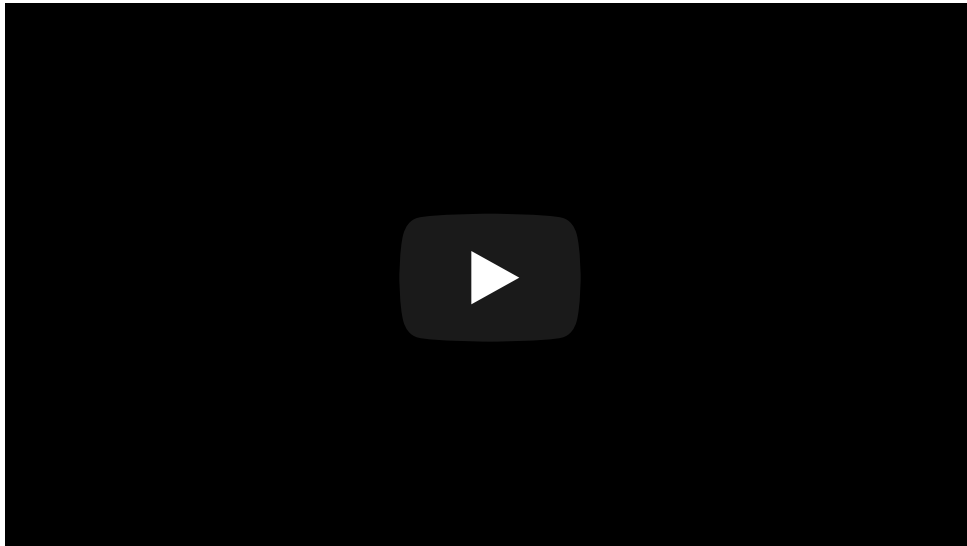





- [How Does it Sound?](#)


You can also check out this video to see a quick overview of the design process. At the end I wire up the amp so you can hear what it sounds like:



THINGS TO DECIDE BEFORE STARTING

Before starting to design your amplifier, you should have an idea about how much *output power* you want to get out of it. Output power is what you'll typically see stated as the Wattage rating of an amplifier. The maximum output power of the LM3886 is 68 Watts, but the actual power you get will depend on your power supply voltage and speaker impedance.

1. Power Quality		6. Audio	
2. Linear Power		7. AC Power	
3. High Voltage		8. Mattress	
4. Power		9. 12 Volt Inverter	
5. Make a PCB		10. Work at Home	



You'll also need to know the *impedance* of your speakers. You should be able to find your speaker's impedance on the back of the speaker or in the user manual.

Finally, you'll need to know your *input voltage*. This is the output voltage of the audio source you'll be amplifying. It may be in the device's user manual, but if not, you can get a rough estimate by playing a 60 Hz pure sine wave (there are apps that will do this) at full volume and measuring the AC voltage between ground and the left or right channel with a [multi-meter](#).

WARNING: THIS PROJECT INVOLVES WORKING WITH MAINS SUPPLY VOLTAGES THAT CAN SERIOUSLY INJURE YOU OR KILL YOU. BE SURE TO TAKE ALL NECESSARY SAFETY PRECAUTIONS, AND NEVER WORK ON A LIVE CIRCUIT!!

DETERMINE THE REQUIRED

POWER SUPPLY VOLTAGE AND POWER

Let's start by figuring out how much voltage and power your amplifier will need from the power supply. These calculations will tell you the correct voltage and VA ratings for the transformer you'll use to power your amp. This step is important because if the transformer's voltage is too low, the output power of the amplifier will be less than what you expected. If the transformer's VA rating is too small, the amplifier might clip or distort the audio at higher volumes.

REQUIRED POWER SUPPLY VOLTAGE

Before you can find the required power supply voltage, you need to calculate the amplifier's *peak output voltage*.

FIND THE PEAK OUTPUT VOLTAGE

Peak output voltage (V_{peak}) is the maximum voltage measured across the amplifier's speaker terminals. Your amplifier's peak output voltage will depend on your desired output power (P_o) and speaker impedance, according to this formula:

$$V_{peak} = \sqrt{2 \times R_L \times P_o}$$

$$R_L = \text{Speaker impedance}$$

$$P_o = \text{Average output power}$$

The amplifier I'm building will be 40 Watts with 6 Ω speakers, so my peak output voltage is:

$$V_{peak} = \sqrt{2 \times 6 \Omega \times 40 W}$$

$$= \sqrt{480}$$

$$= 21.9 V$$

FIND THE MAXIMUM SUPPLY VOLTAGE NEEDED BY THE AMPLIFIER

Now that you've found the peak output voltage of your amplifier, you can calculate the *maximum supply voltage* ($V_{max\ supply}$). This is the voltage the amplifier needs from the power supply to get the desired output power.

To find the maximum supply voltage, take the peak output voltage and add the *voltage drop* (V_{od}) of the LM3886 (4 V). Then factor in your transformer's regulation and the variation in your mains voltage.

Regulation is the increase in output voltage of a transformer when the load isn't drawing current (i.e. the amp stops playing music). Regulation values can usually be found in the transformer's datasheet, but if you don't know your transformer's regulation, a safe value to use is 15%. The regulation of the transformer I'll be using is 6%.

Mains voltages can vary up to 10% depending on your location. It usually peaks late at night when people are asleep and drops in the daytime when more people are awake and drawing current from the power grid.

Use this formula to calculate the maximum supply voltage required by your amplifier:

$$V_{max\ supply} = \pm(V_{opeak} + V_{od})(1 + Regulation)(1.1)$$

$$V_{opeak} = \text{Peak output voltage}$$

$$V_{od} = \text{Voltage drop across LM3886} \Rightarrow 4\text{ V}$$

$$Regulation = \text{Increase in voltage when transformer is unloaded}$$

$$1.1 = \text{Variation in mains voltage (10 \%)}$$

For my 40 Watt amplifier, the maximum supply voltage it needs is:

$$V_{max\ supply} = \pm(21.9\text{ V} + 4\text{ V})(1 + 0.06)(1.1)$$

$$= \pm(25.9 \times 1.06 \times 1.1)$$

$$= \pm 30.2\text{ V}$$

So my power supply will need to deliver a peak

voltage of ± 30.2 V for my amplifier to output 40 Watts into 6 Ω speakers. The \pm symbol indicates that the voltage is +30.2 V on the positive rail and -30.2 V on the negative rail.

The next step is finding a transformer voltage rating that can deliver this maximum supply voltage.

FIND THE MAXIMUM SUPPLY VOLTAGE OUTPUT BY A TRANSFORMER

Keep in mind that a transformer's voltage rating only tells you its *AC voltage* output. The *DC voltage* will be higher after the bridge rectifier diodes on your power supply convert the AC voltage to DC.

To find the maximum DC supply voltage output by a transformer and power supply, take the transformer's AC voltage rating and factor in a 1.41 increase in voltage from the rectifier diodes, the 10% mains supply variation, and the transformer's regulation:

$$V_{max\ supply} = (V_{transformer})(1.41)(1.1)(1 + Regulation)$$

$$V_{transformer} = \text{Transformer voltage rating}$$

$$1.41 = \text{Voltage increase from rectifier diodes}$$











$$1.1 = \text{Variation in mains voltage (10 \%)}$$


$$Regulation = \text{Increase in voltage when transformer is unloaded}$$

I tried the above calculation with a transformer rated at 18 V AC to see if it could supply the 30.2 V maximum supply voltage needed by my amplifier. With an 18 V transformer, I would get a maximum supply voltage of:

$$\begin{aligned} V_{max\ supply} &= (18\ V)(1.41)(1.1)(1 + 0.06) \\ &= 29.6\ V \end{aligned}$$

29.6 V is pretty close to the 30.2 V maximum supply voltage needed by my amplifier, but let's calculate exactly how much output power I'd get with this transformer.

1. Make a PCB		6. Interior Design	
2. High Voltage		7. 12V Switching	
3. Power		8. Power Factor	
4. Audio		9. AC Power	
5. Amplifier		10. Signal Power	



FIND THE OUTPUT POWER FROM A TRANSFORMER'S VOLTAGE RATING

To calculate the output power you'll get from a particular transformer's voltage rating, use this formula:

$$P_o = \frac{(\frac{V_{max\ supply}}{(1+Regulation)(1.1)} - V_{od})^2}{2 \times R_L}$$

$V_{max\ supply}$ = Maximum supply voltage of power supply

V_{od} = Voltage drop across LM3886 $\Rightarrow 4\text{ V}$

Regulation = Increase in voltage when transformer is unloaded

1.1 = Variation in mains voltage (10 %)

R_L = Speaker impedance

Using the maximum supply voltage I calculated for an 18 V transformer (29.6 V), the output power I'll get is:

$$P_o = \frac{(\frac{V_{max\ supply}}{(1+Regulation)(1.1)} - V_{od})^2}{2 \times R_L}$$

$$P_o = \frac{(\frac{29.6\text{ V}}{(1+0.06)(1.1)} - 4\text{ V})^2}{2 \times 6\ \Omega}$$

$$= \frac{(\frac{29.6\text{ V}}{1.166} - 4\text{ V})^2}{12}$$

$$= \frac{(21.4)^2}{12}$$

$$= \frac{458}{12}$$

$$= 38.2\text{ W}$$

38.2 Watts of output power is pretty close to my goal of 40 Watts, so an 18 V transformer will work fine.

REQUIRED TRANSFORMER POWER

Now let's find a minimum VA rating for the transformer that will power your amplifier.

First you'll need to calculate the *total power* (P_{supply}) required by the amplifier. Total power depends on the maximum supply voltage output by the power supply, the amplifier's peak output voltage, and the speaker impedance. The formula to use is:

$$P_{supply} = 2 \times V_{cc} \left(\frac{V_{peak}}{\pi \times R_L} + QPSC_{total} \right)$$

$$V_{cc} = \text{Maximum supply voltage of power supply}$$

$$V_{peak} = \text{Peak output voltage}$$

$$QPSC_{total} = \text{Total quiescent power supply current (from datasheet)}$$

$$R_L = \text{Speaker impedance}$$

I've already calculated the maximum supply voltage of an 18 V transformer (29.6 V), and the peak output voltage of my amplifier (21.9 V). The *total quiescent power supply current (QPSC)* is given in the LM3886's datasheet as 85 mA.

So my 18 V transformer needs to supply the amplifier with at least:

$$\begin{aligned} P_{supply} &= 2 \times 29.6 \text{ V} \left(\frac{21.9 \text{ V}}{\pi \times 6 \Omega} + 0.085 \text{ A} \right) \\ &= 59.2 \times (1.16 + 0.085) \\ &= 59.2 \times 1.25 \\ &= 74 \text{ W} \end{aligned}$$

The total power can now be used to find a minimum VA rating for your transformer.

CONVERT THE TOTAL POWER TO A TRANSFORMER VA RATING

To convert the total power to a transformer VA rating, a general rule of thumb is to multiply it by a factor of 1.5:

$$74 \text{ W} \times 1.5 = 111 \text{ VA}$$

This is the VA required for each channel, so for a stereo amplifier powered by a single transformer, just double it:

$$111 \text{ VA} \times 2 = 222 \text{ VA}$$

Finding a transformer with a VA of 222 will be hard, but you can round-up to the next closest value and use a [250 VA transformer](#) or larger.

DETERMINE THE PROPER HEAT SINK SIZE

The LM3886 needs a heat sink large enough to dissipate the heat it generates or it will quickly become damaged. The minimum size of the heat sink can be found by calculating its *maximum thermal resistance (in °C/W)*.

First though, you'll need to know your LM3886's *maximum power dissipation (Pdmax)*, and the *thermal resistances* in the path heat takes from the chip die to the ambient air.

FIND THE MAXIMUM POWER DISSIPATION

The maximum power dissipation is the limit at which the LM3886's internal SPiKe circuitry is enabled. Sound quality is severely compromised when the SPiKe circuitry is enabled, so to prevent this we need a heat sink with a thermal resistance low enough to dissipate the maximum power dissipated by the LM3886. Pdmax depends on the maximum supply voltage of your power supply and your speaker impedance:

$$P_{dmax} = \frac{(2 \times V_{cc})^2}{2 \times \pi^2 \times R_L}$$

$$V_{cc} = \text{Maximum supply voltage of power supply}$$

$$R_L = \text{Speaker impedance}$$

The maximum supply voltage output from my power supply is ± 29.6 V, and I'll be driving 6 Ω speakers, so my Pdmax is:

$$P_{dmax} = \frac{(2 \times 29.6 \text{ V})^2}{2 \times \pi^2 \times 6 \Omega}$$

$$= \frac{3505}{118.4}$$

$$= 29.6 \text{ W}$$

So my heat sink needs to be able to dissipate 29.6 Watts of power to prevent activation of the SPiKe protection circuit.

FIND THE MAXIMUM THERMAL RESISTANCE OF THE HEAT SINK

There are three resistances to heat flow away from the LM3886:

θ_{jc} : The thermal resistance from the chip's junction (the die) to the case.

θ_{cs} : The thermal resistance of the gap between the chip case and the heat sink.

θ_{sa} : The thermal resistance from the heat sink to the ambient air.

More power will be dissipated when any of the thermal resistances in the path to ambient air are lowered. θ_{jc} is a property of the plastic case enclosing the die, so we can't do anything to lower that.

θ_{cs} can be lowered by using a [thermal paste](#) between the chip and the heat sink. Thermal paste has a thermal resistance of around 0.2 °C/W, but the exact value of the type you use should be available from the manufacturer.

The most effective way to reduce the total thermal resistance is by lowering θ_{sa} with a more efficient heat sink. Heat sinks with a lower θ_{sa} are better at dissipating heat.

The heat sink will dissipate the peak power produced by the amplifier (P_{dmax}) if its thermal resistance (θ_{sa}) is less than or equal to the value calculated with this formula:

$$\theta_{sa} = \frac{[(T_{jmax} - T_{amb}) - P_{dmax}(\theta_{jc} + \theta_{cs})]}{P_{dmax}}$$

T_{jmax} = Maximum junction temperature \Rightarrow 150 °C (from datasheet)

T_{amb} = Ambient temperature

θ_{jc} = Thermal resistance from junction to case

θ_{cs} = Thermal resistance from case to heat sink

P_{dmax} = Maximum power dissipation

The LM3886 is manufactured in two different packages, the LM3886T and the LM3886TF. The LM3886T has a metal flange on the back of the case, and the LM3886TF is all plastic. The plastic case of the LM3886TF gives it a higher θ_{cs} :

- LM3886T: $\theta_{cs} = 1\text{ }^{\circ}\text{C/W}$
- LM3886TF: $\theta_{cs} = 2\text{ }^{\circ}\text{C/W}$

T_{jmax} is the *maximum junction temperature*, or the temperature at the chip's die above which the thermal shutdown circuitry is enabled. The datasheet gives a value for T_{jmax} of $150\text{ }^{\circ}\text{C}$.

T_{amb} is the ambient temperature in $^{\circ}\text{C}$ that the amplifier will be operated at. A typical value for T_{amb} is room temperature ($25\text{ }^{\circ}\text{C}$).

So the maximum thermal resistance (θ_{sa}) of the heat sink for my amplifier with a P_{dmax} of 29.6 W is:

$$\begin{aligned}\theta_{sa} &= \frac{[(150\text{ }^{\circ}\text{C} - 25\text{ }^{\circ}\text{C}) - 29.6\text{ W}(2\text{ }^{\circ}\text{C/W} + 0.12\text{ }^{\circ}\text{C/W})]}{29.6\text{ W}} \\ &= \frac{62.2}{29.6} \\ &= 2.1\text{ }^{\circ}\text{C/W}\end{aligned}$$

So I'll need a [heat sink rated at less than or equal to \$2.1\text{ }^{\circ}\text{C/W}\$](#) to ensure it can dissipate the maximum power produced by the LM3886.

Here's one channel of my amplifier attached to a properly sized heat sink:

CALCULATING THE COMPONENT VALUES

Now that you've calculated the power supply and heat sink requirements, the next step is to find values for the components in the amplifier circuit. I'll be using the schematic below. It's basically the same as the one in the datasheet, but with the optional stability components included:

Note: The components are labeled as they appear in the datasheet.

Here's a diagram of the LM3886's pin layout for your reference:

FIND THE MINIMUM GAIN REQUIRED

The gain can be set to any value above the LM3886's minimum of 10 V_o/V_i , but in order to get your desired output power, it needs to be above a certain minimum value. The minimum gain setting of your amplifier will depend on your input voltage, speaker impedance, and output power according to the formula:

$$A_V \geq \frac{\sqrt{P_o \times R_L}}{V_{in}}$$

$$A_V = \text{Gain} \left(\frac{V_o}{V_i} \right)$$

$$V_{in} = \text{Input voltage}$$

$$R_L = \text{Speaker impedance}$$

$$P_o = \text{Output power}$$

I plan on using an iPhone as the audio source for my amplifier, which has an output voltage of 1 V. The output power I'll get with my transformer and power supply is 38.2 W, and the impedance of my speakers is 6 Ω . So my minimum gain is:

$$A_V \geq \frac{\sqrt{38.2 \text{ W} \times 6 \Omega}}{1 \text{ V}}$$

$$\geq \frac{\sqrt{229}}{1}$$

$$\geq 15.1$$

So I'll need to set the gain to at least 15.1 V_o/V_i if I want 38.2 Watts output power into 6 Ω speakers with a 1 V input voltage.

SETTING THE GAIN

The gain of the LM3886 can be set by changing the values of resistors R_i and R_{f1} . These resistors form a voltage divider that determines the voltage at the inverting input (pin 9) of the LM3886:

Setting the gain too high might cause distortion. Setting it too low might make your amplifier too quiet. A good gain setting that's not too high to cause distortion, but not too low to give you a good range of volume is around 27 to 30 db.

The gain is calculated with this formula:

$$A_V = 1 + \frac{R_{f1}}{R_i}$$

$$A_V = \text{Gain} \left(\frac{V_o}{V_i} \right)$$

$$R_{f1} = \text{Resistance of } R_{f1} \text{ in Ohms}$$

$$R_i = \text{Resistance of } R_i \text{ in Ohms}$$

This gives you the *voltage gain* (V_o/V_i), or the factor of amplification. To convert voltage gain to decibels (db) gain, use this formula:

$$\text{Gain}_{db} = 20 \times \log_{10} \left(\frac{V_o}{V_i} \right)$$

Higher value resistors create more [Johnson-Nyquist noise](#), so it's best to find an R_{f1} / R_i ratio that provides your target gain with low resistor values.

I decided on a gain of around 27 db (22.4 V_o/V_i) for my amplifier. To keep the resistances low, I started out by setting R_i to 1 k Ω . Then I rearranged the gain formula to solve for R_{f1} with a gain of 22.4 V_o/V_i :

$$R_{f1} = R_i(A_V - 1)$$

$$R_{f1} = 1000 \, \Omega (22.4 - 1)$$

$$= 21,400 \, \Omega$$

I'm going to use Vishay-Dale PTF series metal film resistors throughout my amplifier, but the closest

value I could find was 20 kΩ. But using a 20 kΩ resistor for Rf1 would make the gain:

$$\begin{aligned} A_V &= 1 + \frac{20000\ \Omega}{1000\ \Omega} \\ &= 1 + 20 \\ &= 21 \frac{V_o}{V_i} \\ &= 26.4\ db \end{aligned}$$

Which is close enough to 27 db, and above the 15.1 Vo/Vi minimum gain required for my desired output power, input voltage, and speaker impedance.

If you're building a stereo amplifier, you want Ri and Rf1 to have close resistance tolerances. If these resistors vary much between the two channels, the gains will be different and one channel will be louder than the other. Metal film resistors with a tolerance of 0.1% or less are ideal.

BALANCING THE INPUT BIAS CURRENT

After setting the gain, the next step is to balance the input bias currents by choosing values for Rin and Rb:

If the currents at the non-inverting input (pin 9) and the inverting input (pin 10) are different, a voltage will develop between them. This difference in voltage will be amplified as noise.

The inverting input sees the resistance of Rf1 and the non-inverting input sees the resistance of Rin and Rb in series. You already found a value for Rf1 when you set the gain of the amplifier. The values of Rin and Rb are chosen so together they equal the value of Rf1. This will make the current at the non-inverting input equal to the current at the inverting input. To find values of Rin and Rb for a particular Rf1, use this formula:

$$R_{in} + R_b \approx R_{f1}$$

I used the value given in the datasheet for R_b (1 k Ω). So with R_{f1} at 20 k Ω , the value of R_{in} that balances the input bias current for my amplifier is:

$$R_{in} + R_b \approx R_{f1}$$

$$R_{in} \approx R_{f1} - R_b$$

$$\approx 20000 \, \Omega - 1000 \, \Omega$$

$$\approx 19000 \, \Omega$$

You'll probably be able to find a 19 k Ω resistor available with the type of resistors you're using, but 20 k Ω is the closest value I could find with Vishay-Dale PTF resistors so I'll have to settle with that.

SET THE LOW FREQUENCY CUTOFF AT THE AMPLIFIER'S INPUT

C_{in} is in series with the non-inverting input. It's main function is to block any DC present in the audio source, while allowing AC (the audio signal) to pass. DC in the audio source needs to be blocked or it will be amplified along with the audio signal and create a high DC offset at the speakers. This distorts the audio, which we don't want for obvious reasons.

In addition to the DC blocking function, C_{in} and the input resistor (R_{in}) form a high pass RC filter that sets the low end of the amplifier's bandwidth at the non-inverting input:

This filter's *cutoff frequency* (also known as the *-3db point* or *corner frequency*) is the frequency at which the filter starts to work. In a high pass filter, frequencies below the cutoff frequency will be attenuated (muted). In a low pass filter, all frequencies above the cutoff frequency will be muted. We'll use combinations of low pass and high pass filters to set the amplifier's bandwidth and improve stability.

The cutoff frequency (F_c) of this filter can be found

with the equation:

$$F_c = \frac{1}{2\pi R_{in} C_{in}}$$

R = Resistance of R_{in} in Ohms

C = Capacitance of C_{in} in Farads

The equation can be rearranged to find a value of C_{in} for a particular F_c :

$$C_{in} = \frac{1}{2\pi R_{in} F_c}$$

You found the value for R_{in} when you balanced the input bias currents, so all you need now is to choose a cutoff frequency. The lower limit of human hearing is 20 Hz, so the F_c should be well below that to prevent attenuation of bass frequencies. Lower than 2 to 4 Hz is ideal.

I tend to listen to music with lots of bass, so I decided on a fairly low F_c for my amplifier. I started with 1.5 Hz, but you can use higher or lower values if you want. Just be sure to stay well below 20 Hz or the bass will be weak.

With an F_c of 1.5 Hz, the value of my C_{in} needs to be:

$$\begin{aligned} C_{in} &= \frac{1}{2 \times \pi \times 20000 \Omega \times 1.5 \text{ Hz}} \\ &= \frac{1}{188,496} \\ &= 0.0000053 \text{ F} \\ &= 5.3 \mu\text{F} \end{aligned}$$

A 5.3 μF capacitor will be hard to find, but a close value that's fairly common is 4.7 μF . The F_c with a 4.7 μF capacitor would be:

$$\begin{aligned} F_c &= \frac{1}{2 \times \pi \times 20000 \Omega \times 0.0000047 \text{ F}} \\ &= \frac{1}{0.591} \\ &= 1.69 \text{ Hz} \end{aligned}$$

An Fc of 1.69 Hz is pretty close to my desired 1.5 Hz, so a 4.7 µF capacitor should be good.

Since Cin is directly in the path of the audio input signal, the type of capacitor used will have an influence on sound quality. Electrolytics, ceramics, and tantalum capacitors should be avoided. A good quality polypropylene metal film, or even better a polypropylene metal film in oil capacitor will sound best here.

SET THE LOW FREQUENCY CUTOFF AT THE FEEDBACK LOOP

A second high pass filter exists in the feedback loop with Ri and Ci:

The cutoff frequency of this filter should be 3 to 5 times *lower* than the Fc of the Cin\ Rin high pass filter at the input. If the Fc of this filter is *higher* than the input filter, the amplifier will pass low frequencies to the feedback loop that it can't handle. This will create a voltage across Ci and cause DC voltage to appear at the inverting input, which will be amplified and cause distortion. Therefore, the input filter (Cin and Rin) should determine the lower bandwidth frequency of the amplifier, not the feedback loop filter (Ci and Ri).

The input filter defines the low end of the bandwidth, but Ci still has an effect on the bass response. With smaller values of Ci, the bass will be softer and have less punch, but with larger values of Ci, the bass will be tighter and have more impact.

The formula below will give you a starting point for the value of Ci:

$$C_i \geq \frac{\sqrt{2} \times (R_{in} + R_b) \times C_{in}}{R_i}$$

I already found values for Rin, Cin, Rb, and Ri, so the value of my Ci should be greater than:

$$\begin{aligned}
C_i &\geq \frac{\sqrt{2} \times (20000 \, \Omega + 1000 \, \Omega) \times 0.0000047 F}{1000 \, \Omega} \\
&\geq \frac{0.14}{1000 \, \Omega} \\
&\geq 0.00014 \, F \\
&\geq 140 \, \mu F
\end{aligned}$$

Rounding up to the next common capacitance value gives 220 μF . Lets see what the cutoff frequency would be with that. We can use the F_c equation with R_i and C_i :

$$\begin{aligned}
F_c &= \frac{1}{2 \times \pi \times 1000 \, \Omega \times 0.00022 \, F} \\
&= \frac{1}{1.38} \\
&= 0.72 \, Hz
\end{aligned}$$

Now I'll check to see if 0.72 Hz is 3 to 5 times lower than the 1.69 Hz F_c of my input filter:

$$\begin{aligned}
&\frac{1.69 \, Hz}{0.72 \, Hz} \\
&= 2.3
\end{aligned}$$

It's 2.3 times lower. Lets try some larger values for C_i to see if we can't do better than that. Repeating the F_c calculation for a 330 μF capacitor gives 0.48 Hz.

$$\begin{aligned}
&\frac{1.69 \, Hz}{0.48 \, Hz} \\
&= 3.5
\end{aligned}$$

3.5 times lower is okay, but I might be able to do even better with a 470 μF capacitor. Repeating the calculations again with a 470 μF capacitor gives an F_c of 0.34 Hz.

$$\begin{aligned}
&\frac{1.69 \, Hz}{0.34 \, Hz} \\
&= 4.9
\end{aligned}$$

A 470 μF capacitor will set the F_c of my feedback loop filter to 4.9 times lower than the F_c of my input filter. This is great, so I'll use a 470 μF capacitor for C_i .

C_i is also in the audio signal path, so a good quality capacitor should be used. The capacitance will probably be too high to use polypropylene, so you'll likely have to use an electrolytic. However, there are good quality audio grade electrolytics like the [Elna Silmic II](#) or [Nichicon KZ](#) series which shouldn't adversely affect the sound quality.

SET THE HIGH FREQUENCY CUTOFF AT THE AMPLIFIER'S INPUT

R_b and C_c form a low pass RC filter that sets the upper limit of the amplifier's bandwidth at the non-inverting input:

In the datasheet, C_c is shown connected between the non-inverting input and the inverting input. In that configuration, C_c filters radio frequency and electromagnetic interference picked up by the input wires. Unfortunately, it also increases the chance for oscillation. A better way is to connect C_c from the non-inverting input to ground as shown in the image above. That way C_c still filters radio frequencies, but it also acts as a low pass filter that will set the upper limit of the amplifier's bandwidth.

The F_c of this filter should be set well below the lowest radio broadcast frequency in your area, and well above the 20 kHz upper limit of human hearing. Broadcast radio frequencies in the USA are:

- FM: 87.5 to 108 MHz
- AM: 535 to 1605 kHz

I chose to start with an F_c of about 250 kHz. It's well below the lowest AM broadcast frequency (535 kHz), so radio frequencies and most electromagnetic interference should be filtered out. It's also well above the upper 20 kHz frequency of human hearing, so higher audio frequencies won't be attenuated.

To find a value for C_c that gives an F_c of 250 kHz, I'll just rearrange the cutoff frequency formula:

$$F_c = \frac{1}{2\pi R_b C_c} \Rightarrow C_c = \frac{1}{2\pi R_b F_c}$$

$$C_c = \frac{1}{2 \times \pi \times 1000 \, \Omega \times 250000 \, Hz}$$

$$= \frac{1}{1.57 \times 10^9}$$

$$= 6.36 \times 10^{-10} \, F$$

$$= 636 \, pF$$

Since 636 pF is not a common value, I'll round up to 680 pF. With a 680 pF capacitor, the F_c becomes:

$$F_c = \frac{1}{2 \times \pi \times 1000 \, \Omega \times (6.8 \times 10^{-10} \, F)}$$

$$= \frac{1}{4.27 \times 10^{-6}}$$

$$= 234 \, kHz$$

So a 680 pF capacitor will set the upper cutoff frequency to 234 kHz, which is close enough to my desired F_c of 250 kHz. C_c is also in the signal path, so a good quality capacitor should be used. The best dielectric types for audio capacitors in the picofarad range are silver mica or polystyrene.

STABILITY COMPONENTS RF2 AND CF

R_{f2} and C_f dampen resonance in the feedback loop and enhance stability:

R_{f1} , R_{f2} , and C_f form a low pass filter in the feedback loop, but as you can see from the formula in the datasheet, calculating the F_c of this filter is quite complicated:

$$F_c = \frac{R_{f1} \times R_{f2} (s + \frac{1}{R_{f2} \times C_f})}{(R_{f1} + R_{f2}) (s + (\frac{1}{C_f (R_{f1} + R_{f2})}))}$$

The best way to determine values for R_{f2} and C_f is with circuit simulation software such as [LTSpice](#).

That's beyond the scope of this article though, so I'm just going to use the values given in the datasheet.

But if you want to experiment, decreasing the value of C_f will raise the upper F_c of the bandwidth, and increasing the value will lower it.

THE ZOBEL NETWORK

C_{sn} and R_{sn} form a Zobel network at the amplifier's output:

The Zobel network is used to prevent oscillations caused by inductive loads. It also prevents radio frequencies picked up by the speaker wires from getting back into the amplifier's inverting input via the feedback loop.

At high frequencies, the impedance of C_{sn} is very low, so high frequency current is shorted to ground. R_{sn} limits the high frequency current so there isn't a direct short to ground, which could exceed the current limit of the LM3886. Therefore, smaller values of R_{sn} make the Zobel network more efficient at filtering radio frequencies, but it also increases the cutoff frequency, which in turn reduces its effectiveness.

The datasheet gives a value of $2.7\ \Omega$ for R_{sn} , and a value of $100\ \text{nF}$ for C_{sn} . This makes the F_c :

$$\begin{aligned} F_c &= \frac{1}{2\pi R_{sn} C_{sn}} \\ &= \frac{1}{2\pi (2.7\ \Omega) (1 \times 10^{-7}\ \text{F})} \\ &= \frac{1}{0.0000017} \\ &= 589\ \text{kHz} \end{aligned}$$

589 kHz is fairly high, especially since the lowest frequency of AM radio broadcast is 535 kHz. In order to bring this down to a more reasonable level, I decided on using $4.7\ \Omega$ for R_{sn} and $220\ \text{nF}$ for C_{sn} , which lowers the F_c down to 154 kHz:

$$F_c = \frac{1}{2 \pi (4.7 \Omega) (2.2 \times 10^{-7} F)}$$

$$= \frac{1}{0.0000065}$$

$$= 154 \text{ kHz}$$

154 kHz is well above the 20 kHz limit of human hearing, and well below any radio frequencies the speaker wires might pick up.

Since Rsn will need to shunt high currents to ground if the amplifier oscillates, the power rating should be at least 1 Watt. Csn should have low ESR and low ESL, with a voltage rating greater than the rail to rail swing of output voltage. To minimize inductance, locate the Zobel network close to the output pin (pin 4) and keep the traces short.

THE THIELE NETWORK

While the Zobel network reduces oscillations caused by inductive loads, the Thiele network reduces oscillations caused by capacitive loads, usually due to long speaker cables. It also prevents radio frequencies picked up by the speaker wires from getting back into the amplifier's inverting input through the feedback loop.

Inductors have a low impedance to low frequency current and a high impedance to high frequency current. Audio signals are relatively low frequency, so they will flow through the inductor uninhibited. High frequency oscillation current will be impeded by the inductor and be forced to flow through the resistor, which will dampen it.

The datasheet recommends a 10 Ω , 5 Watt resistor in parallel with a 0.7 μH inductor. In a stereo amplifier, there will be one Thiele network per channel. They should be located away from the amplifier's input circuitry to prevent interference from the magnetic fields generated by the inductor. A good location is near the speaker output terminals, separated a bit or at 90° angles to each other to prevent magnetic field

coupling between them.

MAKING THE INDUCTORS

The inductors for the Thiele network are wire wound air core types, made by wrapping enamel coated wire (magnet wire) around a cylindrical object. Since the inductor will be carrying the full output current of the amplifier, the wire should be heavy gauge. 12 to 18 AWG would be good. Use this [Single-Layer Air Coil Calculator](#) to find out how many turns you need for a particular wire diameter and coil diameter.

Or you can calculate the inductance yourself with this formula:

$$L = \frac{d^2 \times n^2}{(18 \times d) + (40 \times l)}$$

L = Inductance in μH


d = Coil diameter in inches

l = Coil length in inches

n = Number of turns

I used [14 AWG magnet wire](#) in my build since it's thick and easy to find. The diameter of 14 AWG is 1.62814 mm. I planned on using a screwdriver shaft with a diameter of 11 mm to form the coil. Entering this information into the inductance calculator, I found I'd need about 12 wraps to get a 0.7 μH inductor.

POWER SUPPLY DECOUPLING CAPACITORS

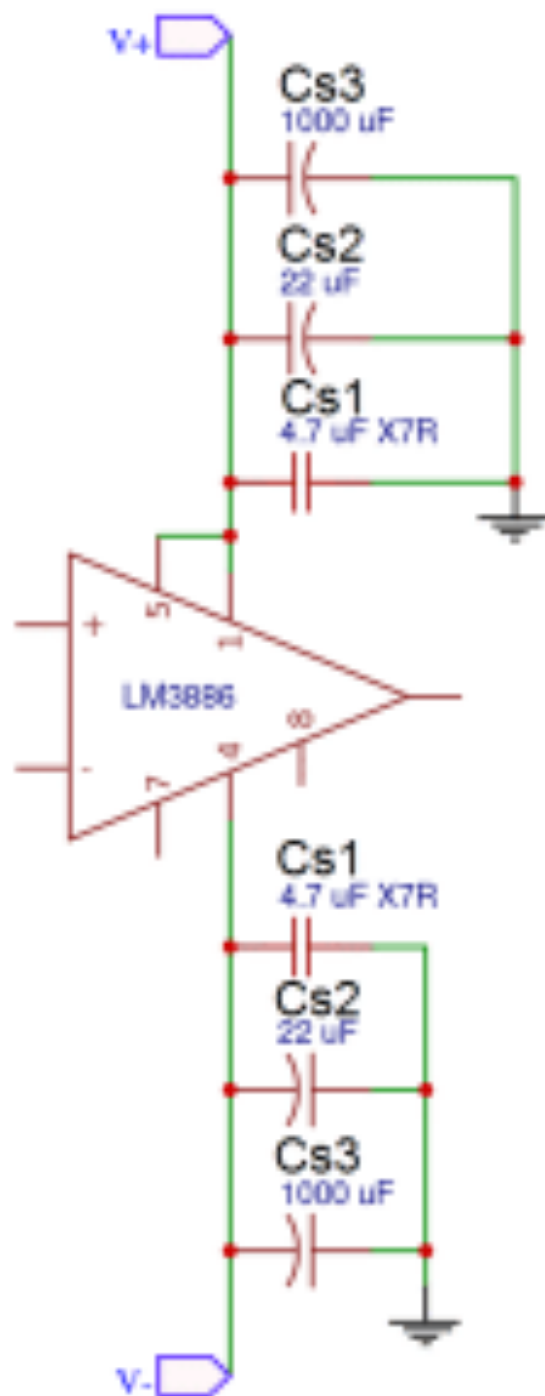

The LM3886 has one negative power supply pin (pin 4) and two positive power supply pins (pins 1 and 5). The negative supply pin needs its own set of decoupling capacitors and the positive supply pins share a separate set of decoupling capacitors.

The large decoupling capacitors provide a lasting source of reserve current when the low frequency output of the amplifier is high. Larger values will improve the bass response. Typical values are between 470 µF and 2200 µF.

The medium value decoupling capacitors supply extra current for mid-frequency output. These should be somewhere between 10 µF and 220 µF.

The small value decoupling capacitors provide current very quickly to help the amplifier output higher audio frequencies. They also filter noise and radio frequency interference in the power

supply.

The decoupling capacitors also compensate for the parasitic inductance and resistance of the power supply wires and traces leading to the the chip's power pins. Inductance and resistance inhibit the flow of current, which increases with longer wires and traces. Since the power supply is relatively far away from the chip, inductance and resistance are a problem. To maximize current flow to the chip, the decoupling capacitors should be placed as close as possible to the chip's power pins.

Capacitors with lower *equivalent series resistance (ESR)* and lower *equivalent series inductance (ESL)* are the best types to use here.

[Research by Tom Christiansen](#) shows that a 4.7 μF ceramic X7R capacitor in parallel with a 22 μF electrolytic and 1000 μF electrolytic has significantly better performance than the paralleled 100 nF, 10 μF , and 470 μF capacitors recommended in the datasheet. That is what I'll be using in my amplifier.

THE MUTE CIRCUIT

R_m , C_m , and D1 form the mute circuit:

When the current flowing out of the mute pin (pin 8) is less than 0.5 mA, the amplifier's output is muted, and when the current is greater than 0.5 mA, the output is un-muted.

To un-mute the amplifier, we need to find a value for R_m so that the current allowed to flow out of pin 8 is greater than 0.5 mA. That can be found with this formula:

$$R_m \leq \frac{|V_{ee}| - 2.6 \text{ V}}{0.0005 \text{ A}}$$

$|V_{ee}|$ = *Absolute value of the negative supply voltage*

For my amplifier running on a $\pm 29.6 \text{ V}$ supply voltage,

$$R_m \leq \frac{29.6 \text{ V} - 2.6 \text{ V}}{0.0005 \text{ A}}$$

$$\leq \frac{27 \text{ V}}{0.0005 \text{ A}}$$

$$\leq 54,000 \Omega$$

So, my R_m will need to be less than 54 k Ω for the current at pin 8 to be greater than 0.5 mA.

R_m and C_m create a time constant that slowly decreases the current at the mute pin when power to the amplifier is shut off, and slowly increases the current when the amp is turned on. The 16 V Zener diode (D1) blocks current flowing out of pin 8 until the diode's breakdown voltage (16 V) has been reached. This produces a soft start/stop effect that gradually increases or decreases the volume instead of abruptly cutting it.

The time it takes the current to ramp up and down can be adjusted by changing the values of R_m or C_m according to the formula for the RC time constant:

$$T = R_m \times C_m$$

$$T = \text{Time in seconds}$$

$$R = \text{Resistance in Ohms}$$

$$C = \text{Capacitance in Farads}$$

For example, if I want a one second long soft start, I could arbitrarily set R_m to 10 k Ω , then find a value for C_m :

$$T = R_m \times C_m \Rightarrow C_m = \frac{T}{R_m}$$

$$C_m = \frac{1 \text{ Second}}{10000 \Omega}$$

$$= 0.0001 \text{ F}$$

$$= 100 \mu\text{F}$$

So setting R_m to 10 k Ω , and C_m to 100 μF will give me a one second long soft start.

THE FINAL SCHEMATIC

Now that we've seen how to calculate the component values, we can start designing the PCB layout and wiring scheme. If you don't want to do all of the calculations we did above, you can use the values I used. Here's the final schematic:

Note: The component labels match the labels on the PCB layout provided below. Click on the image to edit the schematic or change component values.

DESIGNING THE GROUND LAYOUT

The ground layout of your amplifier has a major effect on sound quality. With a properly designed grounding layout, the amplifier's output will be completely silent when the source is connected and no music is playing. With a poorly designed ground layout, the amplifier can produce a very noticeable hum or buzzing sound.

The key to a good grounding layout is to keep low current grounds separate from high current grounds. Low current grounds are the ground feeds to the input circuitry and feedback loop. High current grounds are the ground feeds to the power supply decoupling capacitors, the Zobel network, and the speakers. High currents flowing through the low current ground conductors will create a DC voltage that can show up at the amplifier's input and get amplified as noise.

To separate the low current grounds from the high current grounds, we will create several ground networks:

- *Audio input ground:* Ground for the audio input cable
- *Signal ground:* Ground for the input circuitry – R_{in} , C_c , and R_i/C_i
- *Speaker ground:* Ground for the speakers

- *Power ground:* Ground for the power supply decoupling capacitors, Zobel network, mute capacitor, and the ground pin of the LM3886

These grounds should connect only once at a set of terminals called the *main system ground*. The main system ground is located as close as possible to the reservoir capacitors on the power supply. The main system ground will connect to the mains earth wire via a ground loop protection circuit (explained later), and the amplifier chassis.

The individual ground networks are connected to the main system ground so that higher current grounds are closer to the reservoir capacitors. The diagram below shows how to order the ground connections:

The speaker grounds and audio input grounds are routed directly from their terminals on the chassis to the main system ground.

DESIGNING THE PCB LAYOUT

PCB design also has a major influence on the performance of your amplifier. Below I'll discuss the guidelines I used to design this PCB layout. The PCB is for a single channel, so for a stereo amplifier, you'll need to build two boards:

Note: The components on the PCB layout match the schematic above. You can click on the image above to edit the PCB layout, change the component footprints, and order PCB's.

The PCB was designed with [EasyEDA's](#) online design software. EasyEDA is a full suite schematic and PCB design software/manufacturing service that's free to use and offers great prices on custom PCB manufacturing.

ORDERING PCBs

If you click on the “Fabrication Output” button in EasyEDA’s PCB editor, you’ll be taken to a page where you can [order the PCB](#). You’ll be able to choose the copper thickness, PCB thickness, color, and order quantity:

I ordered 5 boards for \$17.10 USD and they were delivered in about 10 days. The finished boards look great. All of the traces and printing came out very clean and precise, and there were no defects on any of the boards. Here’s one of the PCBs:

PCB DESIGN GUIDELINES

High currents flowing through the power supply and output traces will create magnetic fields that can generate currents in the feedback loop and input traces if they’re routed parallel to each other. This can distort the input signal, so it’s best to keep them far apart or route them at 90° angles. Placing their PCB terminals on opposite sides of the board will make it easier to keep them separate when you route the traces.

Any space between traces of the same circuit will create a loop that can transmit or receive electromagnetic fields. The traces for the power supply feeds and power ground should be routed close together to reduce the loop area. Likewise, the audio input and signal traces should be routed close to each other. An easy way to minimize the loop area is to use ground planes on the bottom layer of the PCB, which I’ve done in this layout.

The power ground and signal ground are the only ground networks on the PCB. Each one has its own electrically isolated ground plane on the bottom layer. Since the power ground carries high currents and the signal ground carries low currents, they’re kept separate until they connect at the main system ground. On the top layer of the PCB, the power supply, output, and Zobel network traces are

routed over the power ground plane. The input and feedback loop traces are routed over the signal ground plane. The traces for the power supply feeds were made very wide to minimize the resistance and inductance.

The feedback loop should be kept as short as possible to reduce the loop area. I trimmed the leads of the feedback resistor (R_{f1}) and soldered it directly to pins 9 and 3 to keep the loop area as small as possible:

Inductance inhibits the flow of current and creates resonance with a capacitor that's in series. Since inductance increases with trace length, it's best to keep all traces as short as possible. This is especially important for the power supply decoupling capacitors, feedback loop, input circuitry, and Zobel network. Keep the components for these circuits right up against the chip's pins so the traces will be short.

We have more tips and tricks on designing PCBs in our [How to Make a Custom PCB](#) article, so check that out if you're interested.

WIRING IT ALL TOGETHER

The LM3886 is a Hi-Fi chip amp, so I used high quality audio grade components for my amplifier:

The total cost came to about \$118 for both channels, not including the chassis, power supply, and wiring parts. You can build it for a lot less with cheaper components if you're on a budget, just be sure to change the component footprints in the PCB layout.

SOLDER AND SOLDERING

Before soldering the components to the PCB, use a piece of fine grit sandpaper to remove any oxidation from the component leads. This will give you a stronger solder joint and better

electrical conductivity.

To hold individual components in place while soldering, use a putty like [Sticky-Tac](#) on the top side of the PCB. Start soldering the smallest components first, and work your way up to the larger components.

Try to avoid the standard 60/40 tin lead solder and use a [63/37 eutectic solder](#) instead. 60/40 solder has a wide melting range, and when it's at the lower end of the range it becomes pasty. If the component moves in the pasty phase, it can create a cold solder joint. The smaller melting range of eutectic solder makes the solder set faster and gives a better electrical connection.

Here's one channel of my amplifier after I soldered the components:

FINDING A CHASSIS

You'll need an enclosure to keep the PCBs and wires contained and to mount the input, output, and power connectors. Metal enclosures are the best type because they shield the amplifier from interference caused by fluorescent lights, radios, and cell phones. Unfortunately it can be hard to find a chassis that fits everything and looks nice too. After a lot of searching, I found a company called Hi-Fi 2000 that manufactures some really nice metal enclosures. Their website is in Italian, but it can be translated to English. I ordered their [330×280 mm Galaxy model with a 10 mm black anodized aluminum front panel](#) and it looks great:

They also do custom drilling and printing, so I had them customize the back panel:

Before you order a chassis, do a test layout of the transformer, power supply, amplifier PCBs, and heat sinks. Then measure the overall dimensions to make

sure the enclosure will fit everything.

WIRING LAYOUT INSIDE THE CHASSIS

After the PCBs have been assembled and you have a chassis, it's time to wire everything together. The wiring layout is just as important as the PCB layout and grounding layout. Use the diagram below as a guide for wiring the various parts together:

Click on the image to view a larger version.

The goal with wiring is to reduce or eliminate electromagnetic interference between high current and low current wires. The audio input wires and signal ground wires are the most sensitive to interference from surrounding magnetic fields.

The power supply wires, speaker output wires, transformer, rectifier diodes, and AC mains wires are a major source of magnetic fields. To reduce interference, keep the audio input and signal ground wires away from these parts or run them at 90° angles if separating them is unavoidable. If you orient the input side of the amplifier PCBs near the input terminals on the chassis, the wires can be kept short and away from sources of interference.

Any space between the wires of the same circuit will create a loop that can transmit or receive electromagnetic fields. To minimize the loop area, the following sets of wires should be twisted together tightly:

- Hot and neutral AC mains wires from the input terminal to the transformer
- AC zero and secondary voltage wires from the transformer to the power supply
- V+, V-, and power ground wires from the power supply to each amplifier PCB
- Speaker output and speaker ground wires from

the amplifier PCB/main system ground to the chassis terminals

- Audio input and input ground wires from the input terminals to the amplifier PCBs

Three power supply wires (V+, V-, and power ground) connect the power supply's DC output to each amplifier PCB. These wires should be thick, as short as possible, and twisted together tightly. I used 14 AWG, but anything larger than 18 AWG should be fine.

Only low currents flow through the input wires and signal ground wires, so they don't need to be heavy gauge. I used solid core 22 AWG, which works well because it can be twisted into a tight coil.

Audio input cables running from the source to the amplifier chassis can pick up interference. If this becomes a problem, you can install a 1 nF capacitor between each input terminal ground and the chassis to filter it.

The mains earth wire should be secured directly to the chassis with a bolt and [ring terminal](#). I'd also use a lock nut or lock washer to prevent it from getting loose. All metal parts of the amplifier (like the heat sinks) should be electrically connected to the chassis to provide a path to earth for any mains voltages that could contact them in the event of a fault.

The main system ground connects to the ground protection circuit (discussed below), which then connects to the chassis. The ground protection circuit can connect to the chassis at the bolt where the mains earth wire is connected to the chassis, or at a separate location.

The two Thiele networks are located close to the speaker output terminals. To prevent interference between the inductors, they should be spaced apart or oriented at 90° angles to each other.

Here's how I installed everything inside my chassis. The right channel PCB is mounted upside down so that the input side of the board is close to the RCA and 3.5 mm input terminals. In this arrangement, the heat sinks provide some shielding from the Thiele networks and the AC wires leading to the transformer:

Click on the image to view a larger version.

THE GROUND LOOP PROTECTION CIRCUIT

GROUND LOOP PROTECTION CIRCUITS MAY BE ILLEGAL IN SOME AREAS. PLEASE CHECK YOUR LOCAL ELECTRICAL CODE OR CONSULT AN ELECTRICIAN BEFORE INSTALLING THIS...

When you connect a powered audio source to your amplifier, magnetic fields from the source's transformer and power supply wires can be coupled into the ground wires of the audio input cables. This is known as a ground loop, and it can create hum in your amplifier's output.

A ground loop protection circuit will break the ground loop current:

Under normal operating conditions, low voltage ground loop currents flow through the resistor (R1) to earth (the chassis). The resistor reduces this current and breaks the ground loop. If a high current fault occurs, the fault current can flow through the diode bridge to earth. Note that the chassis **MUST** be electrically connected to the mains earth wire to prevent mains voltages on the metal chassis in the event of a fault. The capacitor is there to filter any radio frequencies picked up by the chassis.

If a ground loop protection circuit is used, all input and output terminals must be electrically isolated from the chassis. Otherwise, the ground loop

protection circuit will be bypassed entirely by the input/output ground wires that connect to the main system ground.

The ground loop protection circuit can be hard wired, but it's a little neater to mount the components on a PCB. The "PSU 0V" terminal connects to the main system ground. The "Chassis" terminal connects to the chassis:

Click on the image to edit the layout, change component footprints, and [order the PCB](#).

HOW DOES IT SOUND?

The amplifier I built sounds incredibly good. It's the best amp I've ever owned by far. The bass is very deep and clean. You can really feel it. The highs are clear, but not harsh at all. I can hear details in songs that I never knew were there. Trust me, if you build an amp with the LM3886 you will not be disappointed. It definitely lives up to its reputation as a Hi-Fi amplifier. The video at the beginning of the post will give you an idea of what it sounds like.

This should about cover most of what you'll need to build an excellent sounding Hi-Fi amplifier with the LM3886. Due to the length of this post, I decided not to cover the power supply in detail, but I may do so in the future.

If you're interested in building other amplifiers, we also have a tutorial on making a [25 Watt amplifier with the TDA2050](#), and making [10 Watt stereo and bridged amplifiers with the TDA2003](#) as well.

Thanks for reading... If you have any questions on this build, be sure to leave it in the comments below and we'll try to answer it. And be sure to like, share, and subscribe if you found this helpful! Talk to you next time...

Recommended Electronics Engineering Websites:

EasyEDA: Free PCB Design Software. Start to design your own PCB circuit easily.

JLCPCB Prototype: Only \$2 for 10pcs 10×10cm PCBs, 2-3 days delivery.

LCSC Parts: Save 50% on cost, wide selection in-stock, same day shipping.

SHARE:




ABOUT THE AUTHOR




Circuit Basics




RELATED POSTS

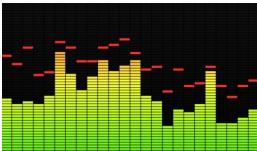

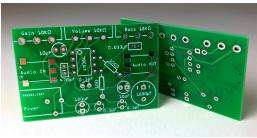
Build a Great Sounding Audio Amplifier (with Bass Boost) from the LM386





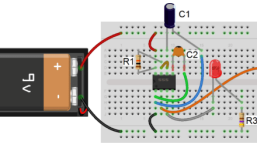



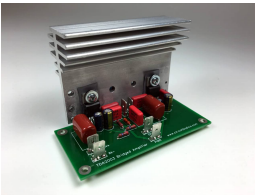



How to Design a PCB Layout




555 Timer Basics – Monostable Mode




A Guide for Building TDA2003 Bridged and Stereo Amplifiers

1. Best SSD Drives		6. Power Quality Analyzer	
2. Natural Gas Price		7. Make a PCB	
3. Power Factor Correction Capacitors		8. Power Car Amplifier	
4. High Voltage Power		9. Power Adapter	
5. Linear Power Supply		10. Signal Power	



44 COMMENTS

1.  **Jeffery Lockmiller** on November 7, 2016 at 5:52 pm
- I use the LM3886 on my biamped mains. A single chip for each tweeter and a parallel pair for the woofers. This setup drives them quite well.

REPLY

2.  **Pero** on November 8, 2016 at 1:59 pm

Hey, great job! thanks for sharing. Cant wait to see post on power supply!

REPLY

3. **Mustafa Kamal** on November 17, 2016 at 11:42 am

Great post and well explained. If possible please post on Power Supply, Speaker Protection, Soft Start and Pre-Amp.
Thanks.....

REPLY

4. **Brian Stover** on January 28, 2017 at 11:34 pm

Love the post. Great detail and explanations of the individual aspects of the circuit. I also really like how you supplied the calculations for determining the size of the components. As others have stated, I'd love to see a followup on the power supply. If not a full post cover it, could you at a minimum post a link to the pcb?

Thanks!

REPLY

5. **marco** on January 29, 2017 at 3:22 pm

Great job, very well explained. Thanks

REPLY

6. **George Riad** on February 3, 2017 at 5:33 pm

I enjoyed every moment of the explanation, Great work and thank you for sharing

REPLY

7. **Vince** on February 7, 2017 at 11:10 am

everything were very well explained. thanks for sharing.

REPLY

8. **Asok Sen** on February 7, 2017 at 6:04 pm

Thank you very much for your detailed explanation, I'm searching for the same.

REPLY

9. **alejandro** on February 10, 2017 at 3:19 pm

Great project; thank you for sharing. The LM3886 is an excellent component and you explained "who to do better".

REPLY

10. **Enrico** on February 14, 2017 at 10:09 pm

Thank you for sharing this.

Shouldn't you also consider the voltage drop on the rectifier diodes, when you calculate the maximum voltage required by the amplifier?

thanks.

REPLY

11. **Wil** on March 4, 2017 at 7:04 am

Thank you for this really great article.

Do you think you could post the exhaustive list, brandd and referenced of the components ?

thanks.

REPLY

Gerontius on April 5, 2017 at 3:33 am

Nice work! I wish I had had this guide years ago when I first

tried building an LM3886 amp. I second the request for component details, such as the voltages of the caps that can't be read, if possible.

REPLY

12. **Martin Arh** on March 6, 2017 at 2:37 pm

Thanks. The best article ever. I learn a lot, specially about grounding.

REPLY

13. **Victor H Faucheret** on March 27, 2017 at 10:28 am

The best post I've ever seen on LM3886. Congratulations! A complete schematic, as well as components values for the power supply will be greatly appreciated, Thank you so much in advance.

REPLY

14. **Luis Peña** on March 30, 2017 at 5:05 am

Thanks for the explanation. I have a question though, if you said your amp will need +-30V, why would a +-18V transformer be enough?

REPLY

Circuit Basics on April 1, 2017 at 2:47 am

The transformer only outputs AC, so the 18V rating is AC voltage. The amp needs about +-30V DC though. When you convert the transformer's AC voltage to DC on the power supply, the voltage actually increases to about 25V due to the bridge rectifier.

REPLY

15. **cd** on March 31, 2017 at 11:43 am

Would be awesome to have links to getting the chosen audio components too.

REPLY

16. **Robert L. Pendergast N5JYW** on April 3, 2017 at 12:38 pm

Beautiful job. Congratulations and thanks for the details.

REPLY

17. **Bob Pendergast** on April 3, 2017 at 12:40 pm

Top quality work.

REPLY

18. **Pietro Di Zinno** on April 3, 2017 at 1:33 pm

True nice complete job! (y)

REPLY

19. **naresh** on April 4, 2017 at 5:17 am

Thank you for sharing this documented design guide for LM3886.

A request .Could you also consider doing a solid state discrete power amp with dual dc power supply.

A pre-amp with tone controls would be also be a welcome.

There are many circuits on the net but again they do not explain any design aspects completely.

REPLY

20. **Aus_Roh** on April 8, 2017 at 7:38 am

A very nice explanation. A lot of effort obviously went into this. Many thanks! Many thanks too for the fantastic links.

You seem to know what you are doing as well as having a lot of experience. Thus, I was wondering if you could state the specifications of your amp, (distortion and noise characteristics) so it can be compared to other LM3886 designs. so see if one needs to improve anything.

designs, so soon one needs to improve anything.

Also, I would try to slide the capacitors away from the heatsink more on the PCB design so that the modules would have a longer life in many years time before breakdowns.

How come you amp isn't picking up hum or the local AM radio station when its not in a shielded box?

Crazy input capacitor!

REPLY

21. **françois** on April 17, 2017 at 12:16 am

Great post!!!!

Thanks.

Just a question: if I want to use a volume control, how should I set the input resistor to limit dc offset due to input bias current?

REPLY

22. **Victor Faucheret** on April 22, 2017 at 5:20 am

thank you so much for your posting of the parts list as well as the power supply schematic and values!!

REPLY

23. **Sascha** on April 25, 2017 at 7:02 am

Thanks a lot for sharing this wonderful job. I will definetly try a build on my own.

Sascha

REPLY

24. **Phil** on May 12, 2017 at 5:34 am

Awesome writeup, many thanks! Quick question, I'm making these amplifiers to work in my car, so I will be using a 12V-30V DC transformer to power it. Should I still include a ground loop protection circuit or is it not needed for this approach?

REPLY

25. **ed linssen** on May 23, 2017 at 9:19 pm

no comment, just want to follow this very nice thread!

REPLY

26. **Darren** on May 25, 2017 at 6:40 pm

I don't know if I am misreading your schematic but it appears that your board silkscreen is mislabeled. The two silver mica capacitors (47pF and 680pF) appear to be reversed in your pictures. the footprint size of the components appears to be reversed if C2 sets the high frequency roll off of the amplifier then this would be the 680pF capacitor (the lager of the two) this is reflected in the picture of your components laid out with labels.

As C13 is used to stabilize the amplifier I would just like confirmation that the parts list and silkscreen are correct.
Thank you.

REPLY

27. **ed linssen** on May 28, 2017 at 8:50 pm

Hi Darren,

I see that on the photograph of the parts family, the names of the two mica C's are reversed.. The 680 is in fact the smaller-, the 47pF is the bigger one!

So the silkscreen is correct....

Success with the build,

Ed

REPLY

28. **José Luiz fonseca** on May 28, 2017 at 11:43 pm

Hi, friend,

I've got the PCB but when I started to put the components , I didn't find the holes for R4. Did you forget it?

I have a transformer that feeds 22V at 7A.. I can use it, no?

REPLY

29. **ed linssen** on May 29, 2017 at 9:17 am

Hi José,

You are supposed to place R4 (20 Ohm) between pins 3 and 9 directly ON the chip.

Good luck,

Ed

REPLY

30. **Konig Heniker** on May 31, 2017 at 10:01 pm

Best tutorial you've ever made and one of the best available online. I hope you'll make more of those overly detailed explanations, amazing knowledge source.

REPLY

31. **Evan** on June 2, 2017 at 3:08 pm

First off - thank you for the great tutorial and the breakdown of each step. As an electrical engineering student, I love getting the chance to truly understand the process of creating the design.

Second, I'm trying to design the amp to go with a pair of Bose Interaudio 4000 speakers, which have a rating of 10-100W and 4-8 ohms. Since they do not have a specific value, but instead a range, should I make the calculations using the higher values, as a worst case scenario or sorts?

Thanks for the help!

REPLY

32. **Liwei Sheng** on June 7, 2017 at 4:55 pm

Wow, best guide about building LM3886 amplifier. I would not call this basics. There are many deep understandings beneath the guide. I like the way you treat ground connections. But I

think three wire transformer output should also do just fine. I would like a kit to same the time to order them. I do not care particular brands of capacitors or any other components as long as their specs meet requirements.

REPLY

33. **dimitris** on June 10, 2017 at 7:38 am

Excellent post! I would like to ask some questions. Firstly , if we want a volume control for this amplifier, how we will achieve it?

Second is there any need for preamp as my audio source would be a laptop or a smatphone.

REPLY

34. **IBRAHIM DILEK** on July 9, 2017 at 11:11 am

Hello , this is a real complete guide for building a high quality amplifier. However I am almost a new graduate of Electrical Engineer and not sure if I can handle the processes. Anyone has any idea on how to be qualified in order to build this amplifier without major mistakes ? Thank you in advance.

REPLY

35. **Raf** on July 16, 2017 at 12:32 pm

Hello Circuit Basics. I really enjoyed reading this awesome guide! I would like to know if there is a way to buy the power supply PCB instead of making it from scratch. Thank you.

REPLY

36. **Robert** on July 21, 2017 at 9:09 am

Hi, I really enjoyed reading this ! I don't have the patience to start this project can you advise me on where to find a really good lm3886 assembled board. also have an 8 ohm load and looking for Lm board with at least 80w/ channel.

Thanks again,
Rob nyc

37. **nheco** on July 22, 2017 at 4:37 pm

Congratulations for the excellent post!

I assembled the circuit exactly like the one in the guide, with the following changes in the PSU: 24-0-24 250 VA transformer and 4x 10000 uf 50V, having + -32.8 volts dc. In the rest everything is equal to the circuit. The sound is fantastic, however I can not reach it but the power is far from expected. What could be wrong?

Can you help please.

Thank you.

Nheco

REPLY

38. **Simon Jones** on August 2, 2017 at 4:11 pm

Thank you for your excellent work on this guide. I think you've completed the most comprehensive and understandable post on this subject. I can't thank you enough.

REPLY

39. **Chris** on August 5, 2017 at 2:38 pm

Hi! This is really a fantastic guide for a newbie like myself. I would also like to see a follow up post with details on the power supply. And I have a few questions:

Is there any reason why the input capacitor C1 has such a huge voltage rating well above the theoretical maximum of 60.4V from the positive to the negative rail of the power supply? Or is it just because the part is only manufactured like that by Mundorf?

If the latter: Are there any benefits (audio signal quality or other reason) with axial capacitors with such big plates? I was thinking of using one of the smaller WIMA MKP 4 series capacitors for C1. Those are also metalized polypropylene film capacitors, but with a smaller footprint and lower voltage ratings. The drawback is a bigger tolerance (10%), but they are dirt cheap compared to the Mundorf monster cap used here

(WIMA MKP4F044706F00KSSD is about 1/7 of the price and way easier to find where I live).

And lastly a tip/request/suggestion for your CSS:

Could you please add a print stylesheet to the website, where all the unnecessary stuff (navigation, newsletter subscription, social links, footer, etc) is hidden and the content column has full width?

Also, older versions of Firefox have problems when parts of the page are not “display: block”. On this web site it’s the #content-area DIV that is set to “display: flex”, that causes Firefox to print only the header on the first page, then whatever part of the article fits on the second page, followed by third page with just the footer. All other (47) pages of the article and the comments are hidden.

You could even add a DIV at the top of the web page with a .print-only class attribute, that is invisible when the page is viewed on a screen/tv, but would be included in the printed version. In there you could put things like a publishing date and a copyright notice, keywords, a table of contents, (social link) URLs written in full as normal text instead of just blue words in the article, etc.

REPLY

40. **Jimmy George** on August 23, 2017 at 12:00 pm

I made an amp with LM3876 in 2015. From then on, I have been trying to improve its performance by making modifications. In addition, I wanted to publish a systematic article with instructions on that. However, due to lack of deep knowledge in electronics, the project was lagging behind.

Surprisingly, while searching for “Negative Feedback” of amps, I came here. This is amazing. Though I have no expertise in Physics, was able to understand the technical things in this article. This is far far better than I wanted to publish, or would say – THE BEST. Awesome job, guys.

REPLY

41. **Dave** on September 6, 2017 at 10:35 pm

Thanks for all the hard work. I noticed that in the schematic you have a 100nF cap (Csn). And in the photo under Wiring It All Together, there is a polypropylene cap labelled as a 100nF cap (I assume this is Csn). You explain in the tutorial (and as the actual photo of the cap shows) the actual value of the polypropylene is .22uF. Could you update this info. Thanks.

REPLY

42. **Judah** on October 4, 2017 at 10:53 am

Thanks a lot for this awesome project. This is my first and through the detailed explanation, I'm well able to understand almost all of it.

I have a question though. For the power supply circuit, how can I connect diodes and capacitors to safely give the required voltage and do away with the transformer.

Thanks in advance.

REPLY

LEAVE A REPLY

Your email address will not be published. Required fields are marked *

COMMENT

NAME *

EMAIL *

WEBSITE

☒ Send new posts to my inbox.

☐ Notify me of follow-up comments by email.

POST COMMENT

